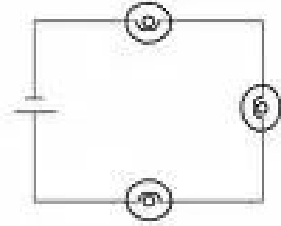


## Circuitry Pre/Post-Assessment

NAME: \_\_\_\_\_

1. What kind of circuit is shown below?

- a. series
- b. parallel




5. Electrical wiring in homes use \_\_\_\_\_ circuits.

- a. series
- b. parallel
- c. overloaded
- d. voltage

2. What kind of circuit is shown below?

- a. series
- b. parallel

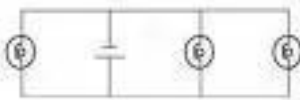

6. Which of the following could be used as an insulator?

- a. rubber
- b. wire
- c. metal bolt
- d. metal

3. The pathway for electrical current is called a

- a. highway
- b. electric route
- c. circuit
- d. path

7. A continuous flow of electrons is a

- a. current
- b. conductor
- c. resistance
- d. insulator

4. Objects that allow electrical current to flow are called \_\_\_\_\_.

- a. circuits
- b. nonconductors
- c. batteries
- d. conductors

8. The unit that measures a battery's strength is called \_\_\_\_\_.

- a. volt
- b. conductor
- c. circuit
- d. current